Instructions for filling the sheet:
- Don't fold the sheet. Use only ball pen. Read the given paragraph carefully.
- Below the paragraph, you will find questions with blanks.
- Use the Answer Bank provided to fill in the blanks with the most appropriate word(s).
- Each word/phrase from the Answer Bank can be used only once, unless stated otherwise.
- Write only the correct word(s) in the blank space provided.
- Spelling errors may result in the loss of marks.
- Do not use words that are not in the Answer Bank.
- **Only use *UPPER CASE CAPITAL LETTER ALPHABETS* in the boxes.**

Admission number

Student Name

Class **Section** **Date (ddmmyyyy)**

Paragraph: When resistors are connected in series, the total resistance is the sum of individual resistor values. This means that each resistor must be sized to handle the current flowing through it without exceeding its maximum capacity. Adding more resistors in series increases the total resistance and reduces the overall current flow.

Answer bank: CURRENT, RESISTORS, SERIES, VALUES, TOTAL, INCREASES, MAXIMUM, REDUCES

Q1. This means that each resistor must be sized to handle the

____ flowing through it without exceeding its maximum capacity.

Q2. When resistors are connected in

____, the total resistance is the sum of individual resistor values.

Q3. Adding more resistors in

____ increases the total resistance and reduces the overall _____ flow.

Q4. The total

____ is the sum of individual resistor _____.

Q5. This means that each resistor must be sized to handle the

____ flowing through it without exceeding its maximum _____.

Q6. The addition of more resistors in series does not affect the

____ value of a single resistor.

Q7. Adding more resistors in series

____ the total resistance and reduces the overall _____ flow.

Q8. The total

____ is reduced by adding more resistors in series.

Q9. Each resistor must be sized to handle the

____ flowing through it without exceeding its maximum _____.

Invigilator's Signature: _____

Student's Signature: _____