Instructions for filling the sheet:

- Don't fold the sheet. Use only ball pen. Read the given paragraph carefully.
- Below the paragraph, you will find questions with blanks.
- Use the Answer Bank provided to fill in the blanks with the most appropriate word(s).
- Each word/phrase from the Answer Bank can be used only once, unless stated otherwise.
- Write only the correct word(s) in the blank space provided.
- Spelling errors may result in the loss of marks.
- Do not use words that are not in the Answer Bank.
- **Only use *UPPER CASE CAPITAL LETTER ALPHABETS* in the boxes.**

Admission number

Student Name

Class **Section** **Date (ddmmyyyy)**

Paragraph: When resistors are connected in parallel, each resistor experiences the full voltage of the circuit. The combined resistance of a system of resistors in parallel is less than the individual resistances would be if they were connected in series. This occurs because each resistor carries only a portion of the total current, and the total current is greater than it would be for each resistor alone. The total resistance of the system is determined by the reciprocal of the sum of the reciprocals of the individual resistances.

Answer bank: SERIES, VOLTAGE, CURRENT, PORTION, RECIPROCAL, TOTAL, RESISTORS, SYSTEM

Q1. Circuits with resistors connected in _ have a combined resistance less than the sum of the individual resistances.

Q2. The full _ is experienced by each resistor when they are connected in parallel.

Q3. A _ of the total current is carried by each resistor in a parallel circuit.

Q4. The _ of the system is determined by the reciprocal of the sum of the reciprocals of the individual resistances.

Q5. In a parallel circuit, the total _ is greater than it would be for each resistor alone.

Q6. Each resistor experiences only a _ of the total current.

Q7. A _ circuit has a combined resistance that is equal to the sum of the individual resistances.

Q8. The _ of the system is less than the sum of the individual resistances when resistors are connected in parallel.

Q9. Circuits with resistors connected in _ have a greater total _.

Invigilator's Signature: _____ Student's Signature: _____